
## Numerical Analysis

## Homework 3. Resistor Networks


Due: March 21, 2017

Please formulate and solve the following resistor network problems.

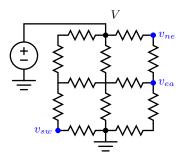
1. Assuming each resistor is 1 K $\Omega$  and the voltage, V, is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



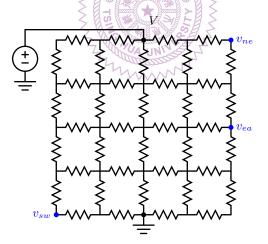
2. Assuming each resistor is 500  $\Omega$  and the voltage, V, is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



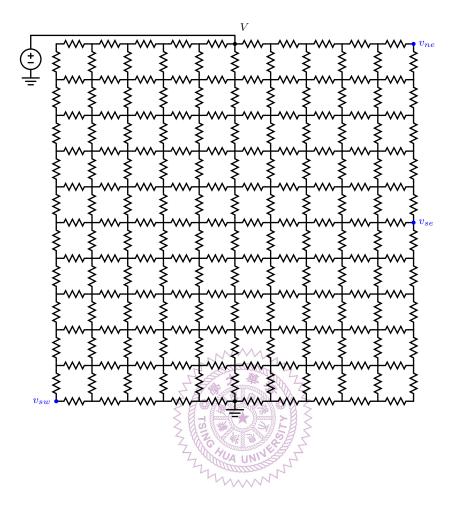3. Assuming each resistor is 200  $\Omega$  and the voltage, V, is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



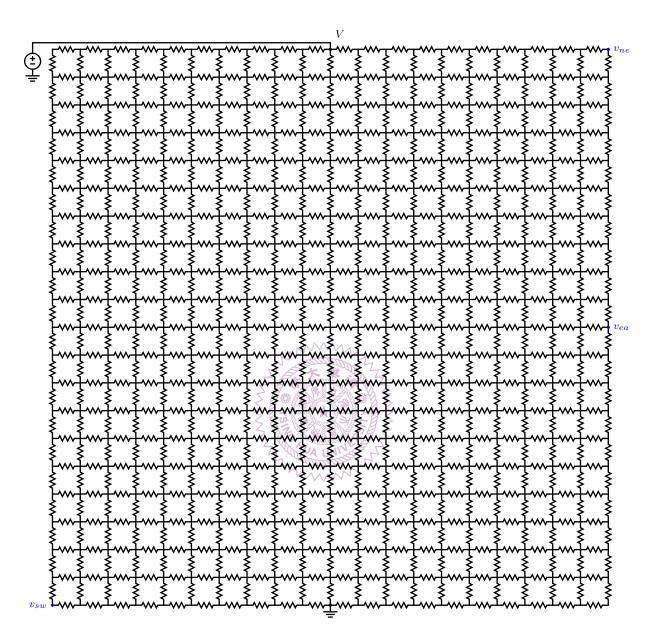4. Assuming each resistor is 100  $\Omega$  and the voltage, V, is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



- 5. Assuming that the resistor mesh has 40 resistors per side and each resistor is 50  $\Omega$ . The 1-Volt voltage source is connected to the center of the north side and the center of south side is grounded.  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$  is the voltage value for the north-east corner, center of east side and south-west corner, respectively. Please find the equivalent resistance and the voltages of those three nodes.
- 6. Assuming that the resistor mesh has 50 resistors per side and each resistor is 40  $\Omega$ . The 1-Volt voltage source is connected to the center of the north side and the center of south side is grounded.  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$  is the voltage value for the north-east corner, center of east side and south-west corner, respectively. Please find the equivalent resistance and the voltages of those three nodes.

7. Please state your observations after solving all six questions.

## Notes.

1. For this homework you need to turn in a C++ program that solves the resistor network problem for question 6. If you program is parametrized then it can solve for all 6 problems using command line arguments. For example,

## \$ ./a.out 10

to solve question 3 that each linear dimension has 10 resistors. If your program is not parametrized, then turn in the one that solves question 6. Name your program hw03.cpp.

- 2. A pdf file is also needed. Please name this file hw03a.pdf.
- 3. Submit your files on EE workstations. Please use the following command to submit your homework 3.
  - $\sim$  ee407002/bin/submit hw03 hw03a.pdf hw03.cpp MAT.h MAT.cpp VEC.h VEC.cpp where hw03 indicates homework 3.
- 4. Your report should be clearly written such that I can understand it. The writing, including English grammar, is part of the grading criteria.