

Numerical Analysis
homework 11: Diode Networks

Due on Tuesday, May 16, 2017

102061149 Fu-En Wang

1 Introduction

To calculate the current of a diode, the formula is:

$$i_d = I_s(e^{\frac{v_d}{\phi}} - 1) \quad (1)$$

$$\phi = \frac{\phi_0 T}{300} \quad (2)$$

where I_s is 1 Amps, ϕ_0 is 0.026 Volts and v_d is the cross-voltage of diode.

In this homework, we will build a Non-linear System to analyze the following diode network.

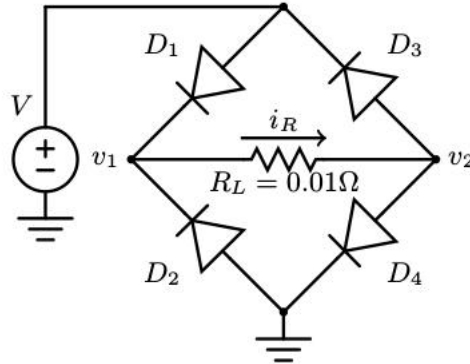


Figure 1: Simple Diode Network

To build a robust function to solve any non-linear system, I use **Finite Difference Approximation** to calculate Jacobian matrix

$$\frac{\partial F}{\partial x} = \frac{F(x+h) - F(x)}{h} \quad (3)$$

1.1 Problems

In this homework, we need to solve two problems:

1. With temperature fixed at 300k, find v_1 , v_2 , i_{D1} , i_{D2} , i_{D3} , i_{D4} and i_R when $V = -1.0, -0.98, \dots, 1$ Volt.
2. With initial temperature is 300k and v_1 , v_2 are 0 Volt. Find v_1 , v_2 , i_{D1} , i_{D2} , i_{D3} , i_{D4} , i_R , T_{D1} , T_{D2} , T_{D3} , T_{D4} when $V = -1.0, -0.99, \dots, 1$ Volt. And the temperature will increase with this formula:

$$T_d = 300 + 2 * i_d * v_d \quad (4)$$

Because Newton Method is sensitive to the initial guess, so we can start solve the system at $V = 0$ and then solve $V = 0.02$ which initial guess is the result from $V = 0$ and so on.

2 Implementation

Algorithm 1 Cyclic Jacobian Updates

```
Given initial guess  $x_0$  and  $\text{tol}$ 
 $k = 0$ 
while  $\text{error} > \text{tol}$  do
    evaluate  $F(x_0)$ 
    if  $k \% p == 0$  then
        calculate Jacobian matrix
    end if
     $J_F(x_0)\delta x = -F(x_0)$ 
     $x_0 = x_0 + \delta x$ 
     $k++$ 
     $\text{error} = \|F(x_0)\|$ 
end while
```
